



**Engineering**

# **Basic Electricity Concepts**

**April 9, 2020**



## 9-12/ Engineering

### Basic Electricity Concepts: [April 9, 2020]

#### **Objective/Learning Targets:**

1. Discuss basic electricity relationships
2. Analyze the differences between real circuits and the simulated ones
3. Build circuits from schematic drawings

# Basic Electricity Concepts

## Electrical Circuit


A system of conductors and components forming a complete path for current to travel

### Properties of an electrical circuit

Concept	Measurement	Symbol	Formula
Voltage	Volts	V	V
Current	Amperes	A	I
Resistance	Ohms	$\Omega$	R

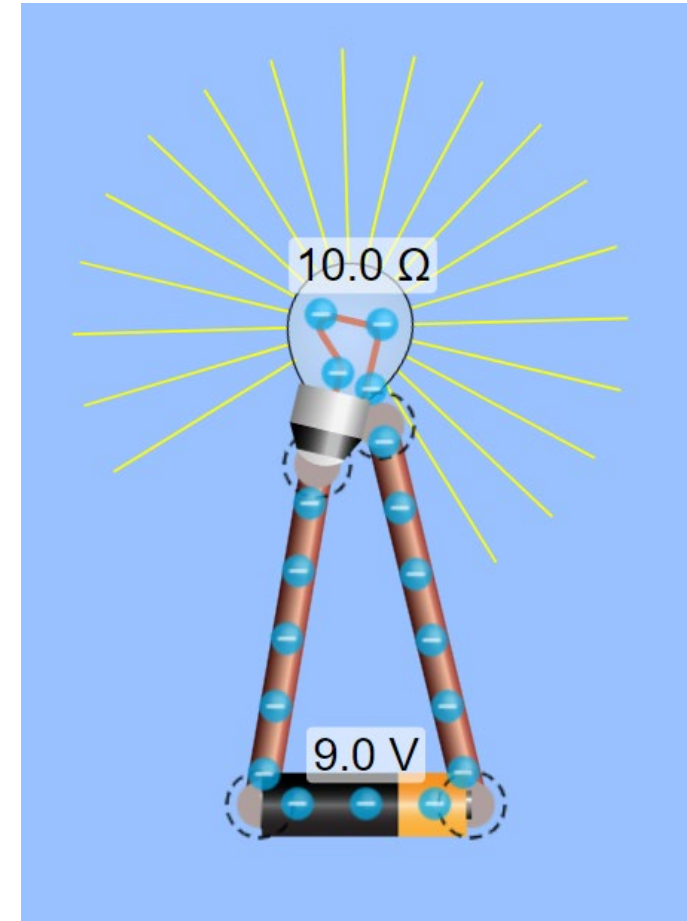
# Current

- The flow of electric charge
  - Measured in Amperes (A)
- [See Current in Action HERE](#)
- [Use this link and press play to enter a free simulator.](#)
- Select intro and build this simple series circuit. You need a battery, a light bulb, and 2 wires. Click the selection in the top right for labels and values.



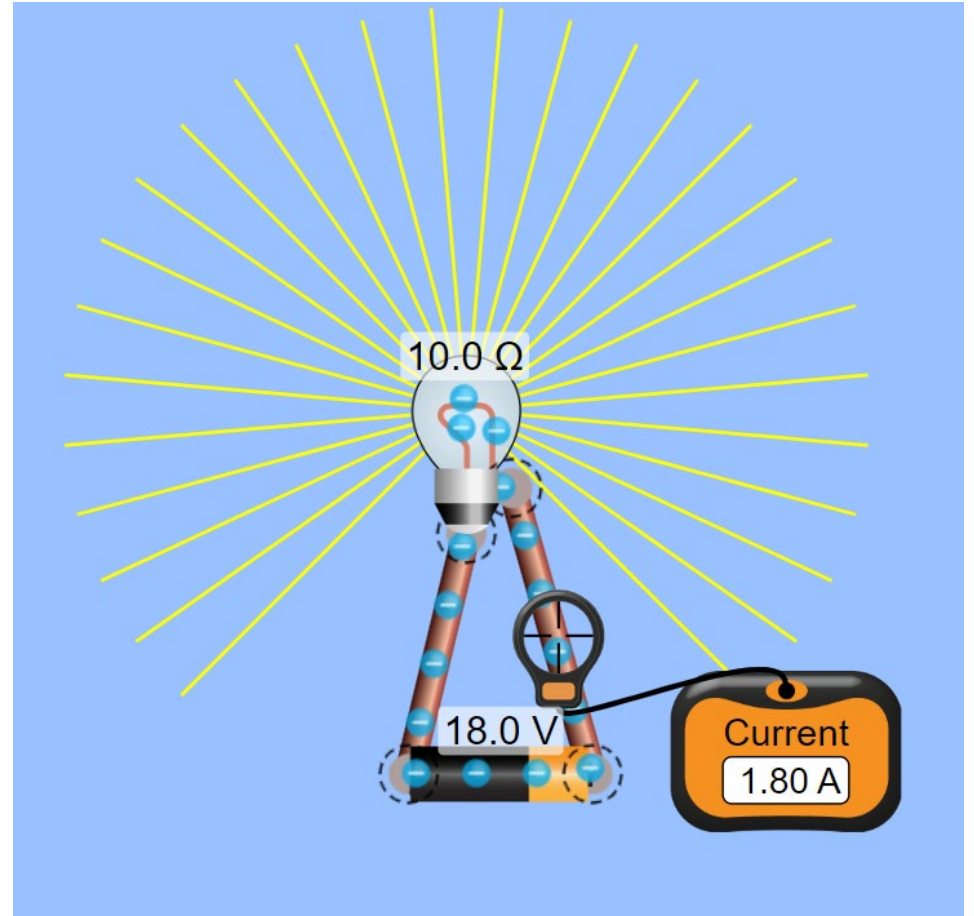
# Simulator

- A simulation is a computer program that mimics real life to test potential results. The simulator we are using is very basic but allows you to do testing to understand the concepts.
- Add the Ammeter to the circuit to take a current reading of the circuit.
- Change the voltage to see the current also change.
- What do you observe about the relationship between current and voltage?



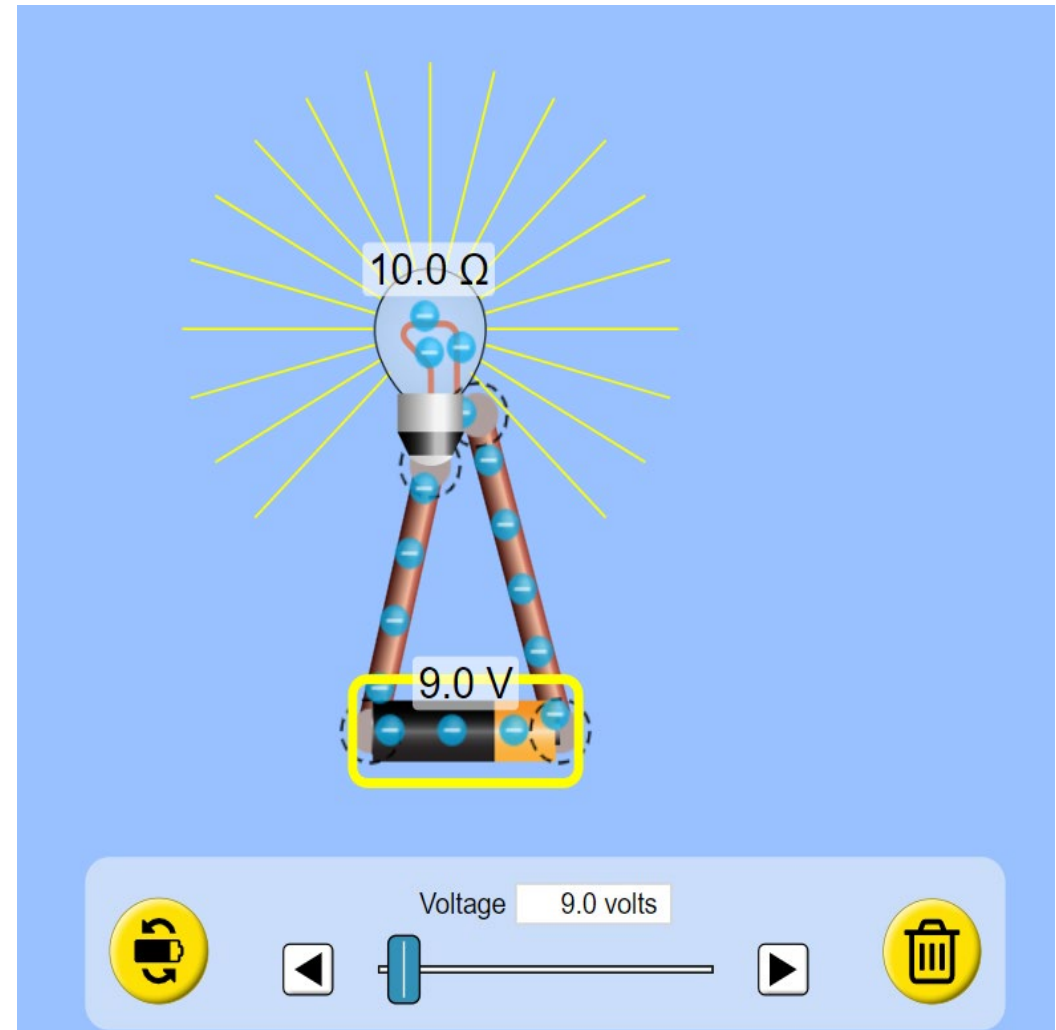
# Current

- [Use this link and press play to enter a free simulator.](#)
- Increase the voltage of the battery by clicking the battery and adjusting the slider.
- What did you observe?
- How does that relate to the video you watched?
- How does the light bulb respond?
- What about the electrons?



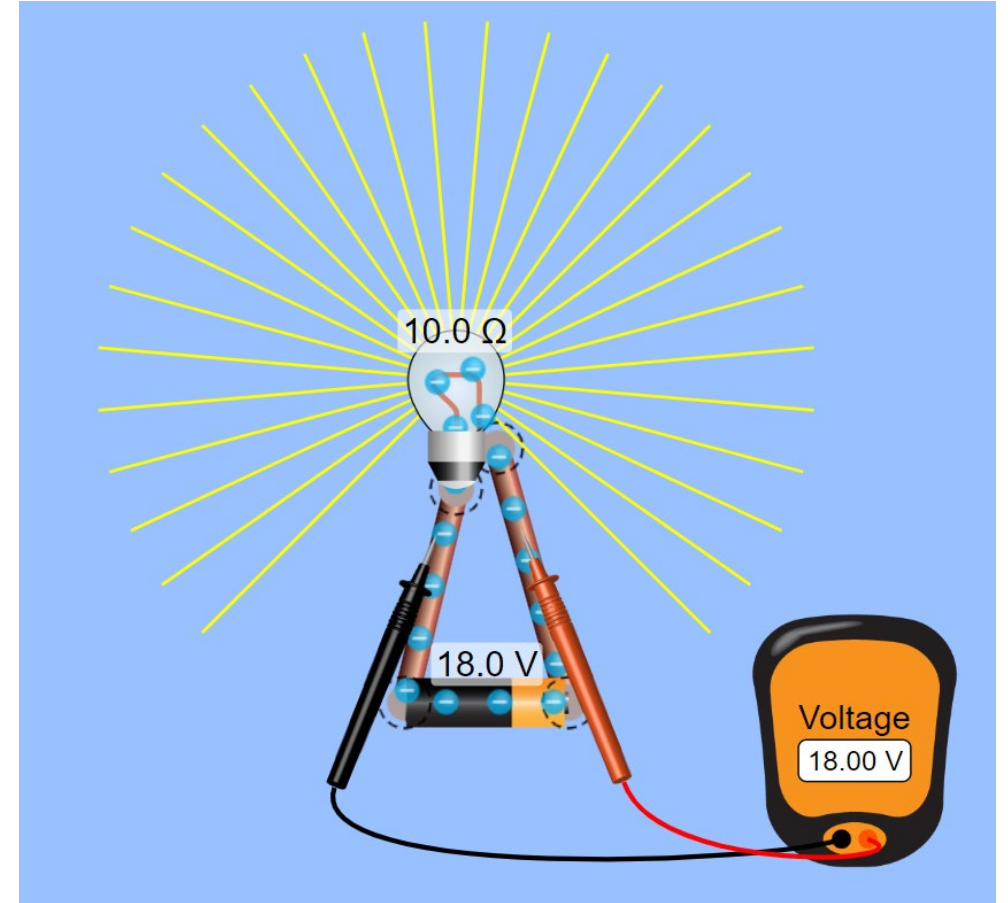
# Voltage

- The force (pressure) that causes current to flow
  - Measured in Volts (V)
- [See Voltage in Action HERE](#)
- Place the multimeter into the simulation
- Do the measurements match the circuit values?
- What happens if you reverse your leads?


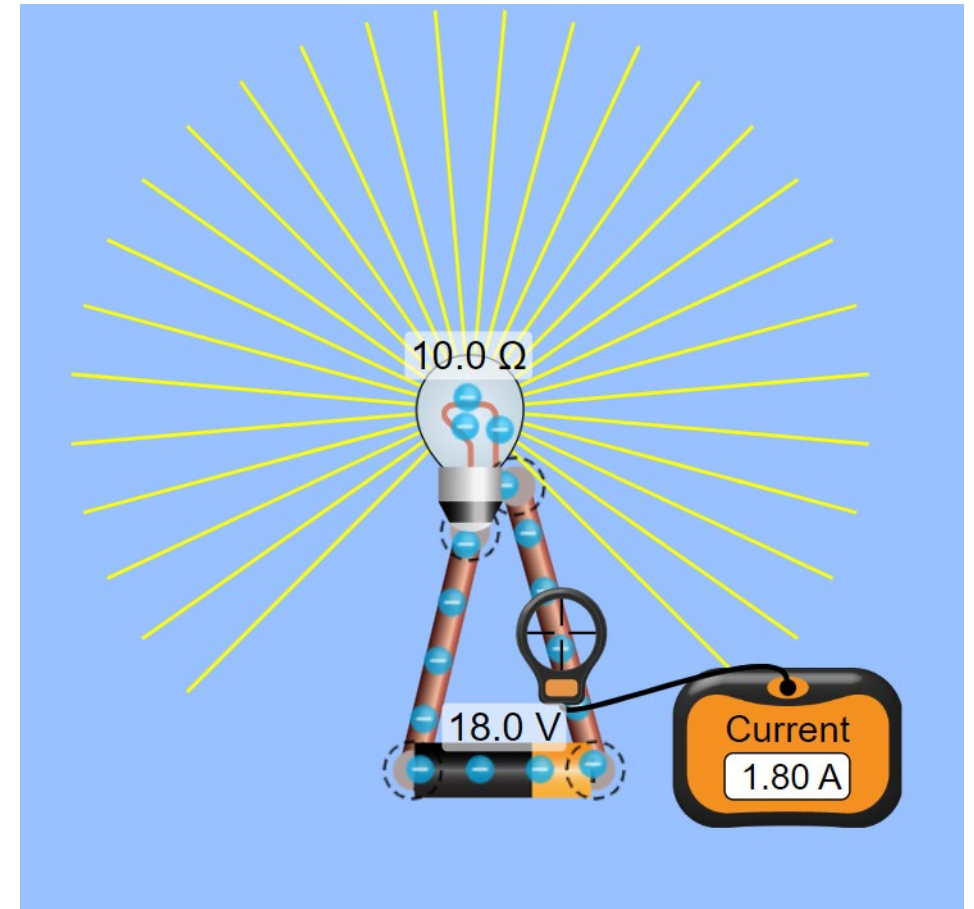
# Resistance

- The opposition of current flow
  - Measured in Ohms ( $\Omega$ )
  - Resistance slows current down
- [See Ohm's Law in Action HERE](#)
- Set the circuit up this way and change the value of the lightbulb.
- What do you observe?
- What do the measurements show?
- Can you make the circuit catch on fire?





# Relationships of Electrical Properties

## Ohm's Law

- Ohm's Law is the mathematical relationship between current, voltage, and resistance.
- If you know two of the three quantities, you can solve for the third quantity.

$$V=IR$$


$$I=V/R$$

$$R=V/I$$

Concept	Measurement	Symbol	Formula
Voltage	Volts	V	V
Current	Amperes	A	I
Resistance	Ohms	$\Omega$	R

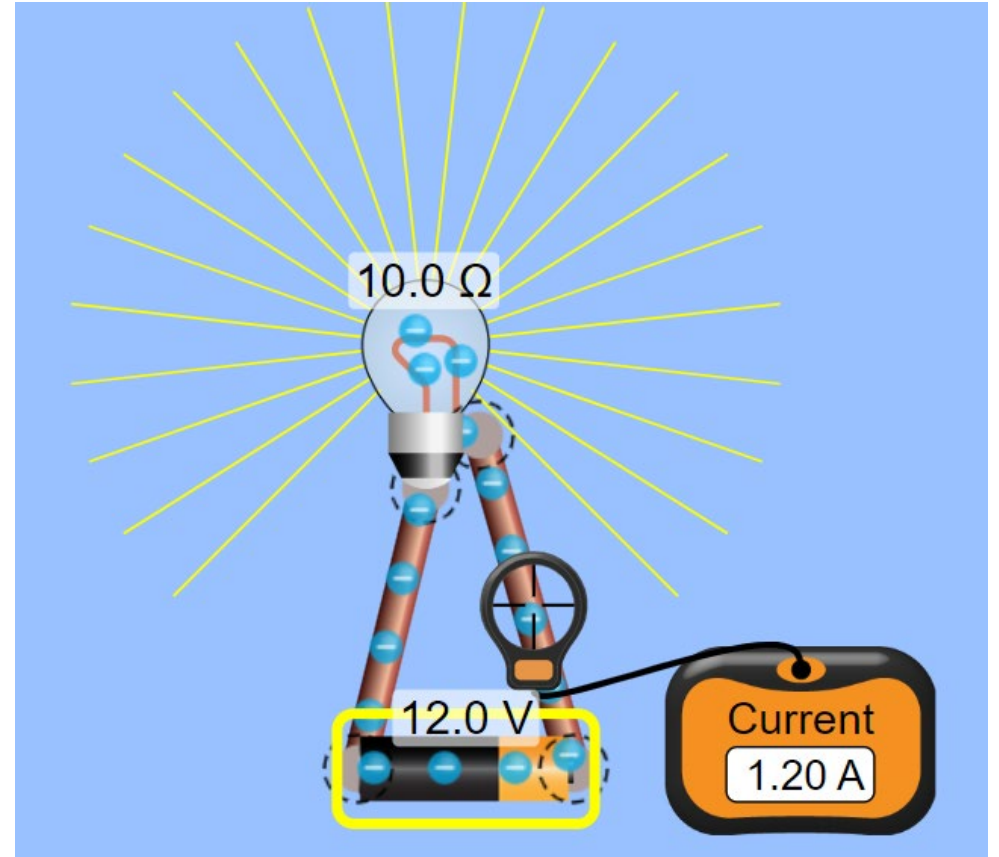
# Ohm's Law

- Lets solve for the circuit to the left assuming we do not know the voltage.
- $V = IR$
- $V = 1.2A * 10\Omega$
- $V = 12V$



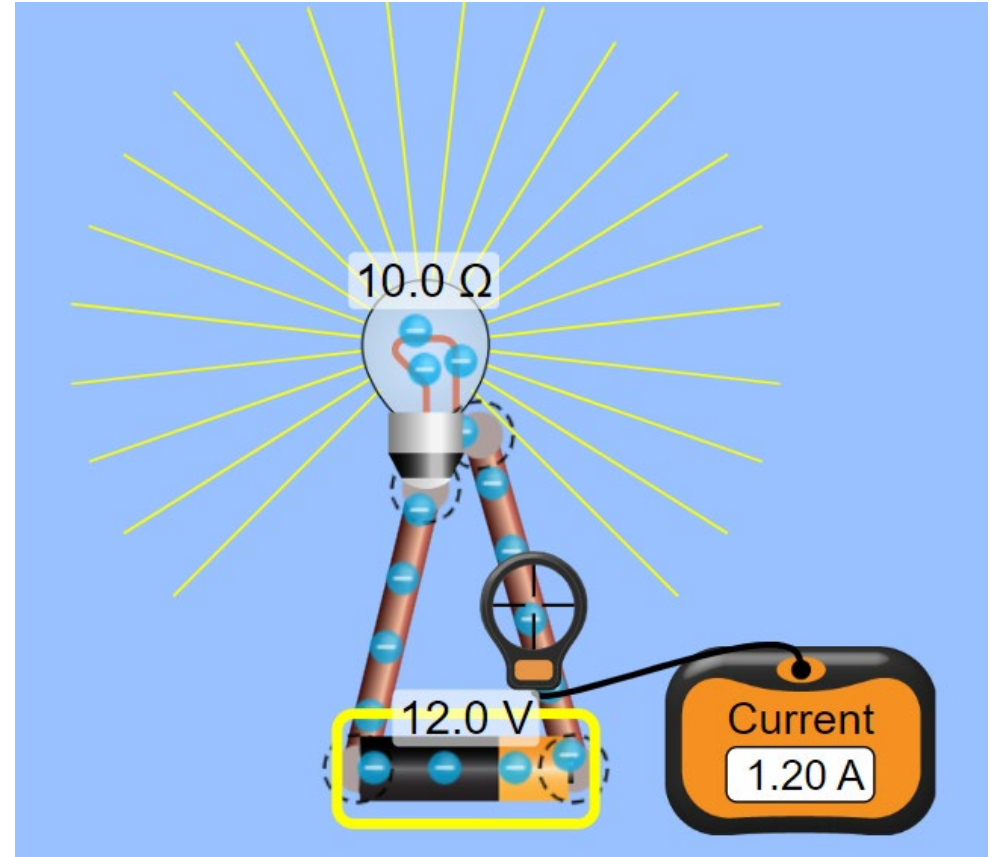
# Ohm's Law

- Your Turn
- Solve for current and resistance
- $I = V \div R$
- $R = V \div I$



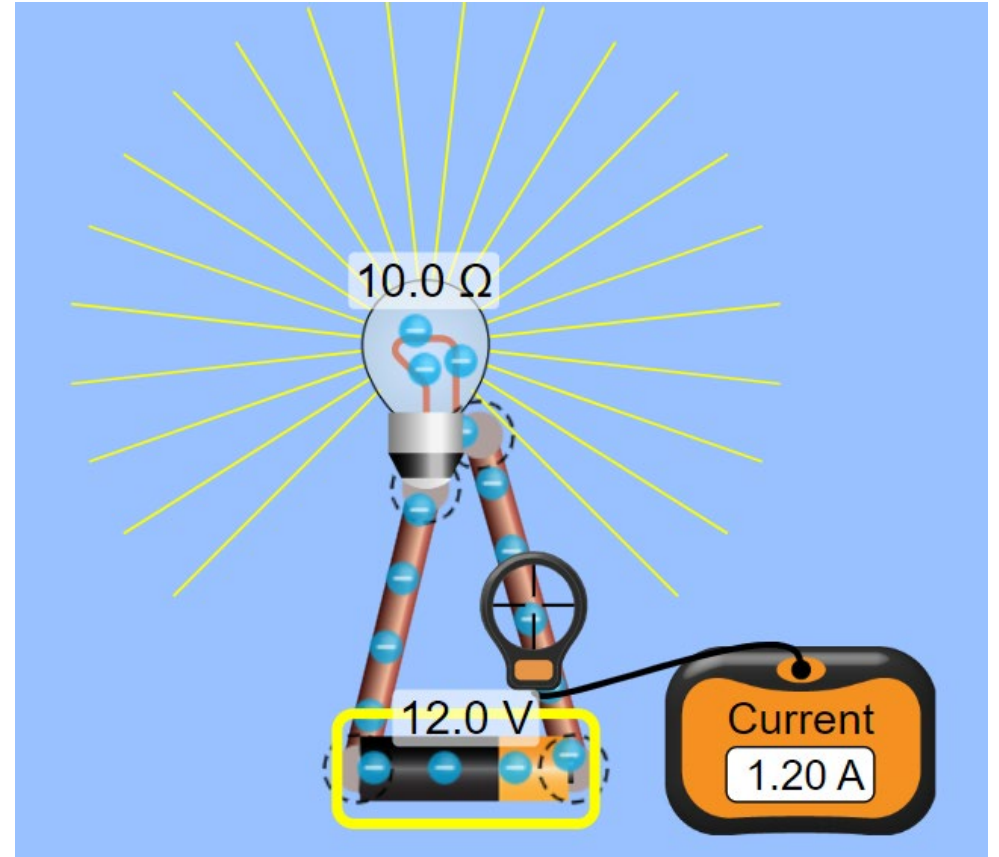
# Ohm's Law

- Your Turn
- Solve for current
- $I = V \div R$
- $I = 12V \div 10\Omega$
- $I = 1.2A$


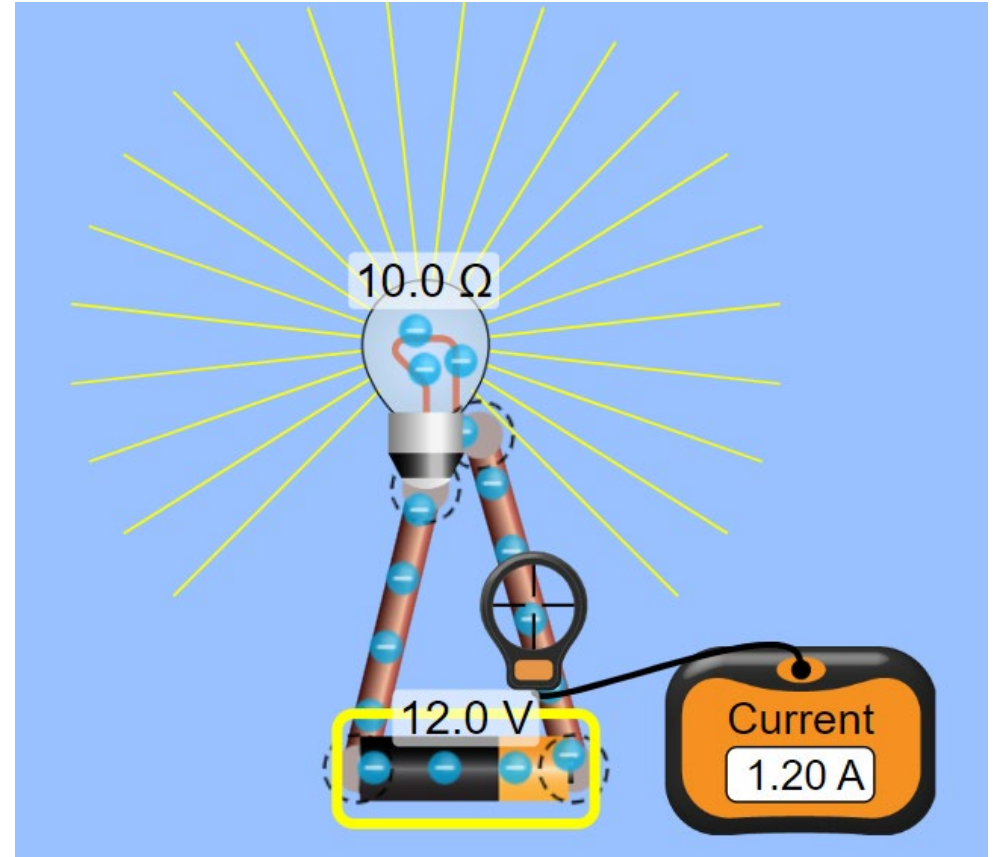
# Ohm's Law

- Your Turn
- Solve for Resistance
- $R = V \div I$
- $R = 12V \div 1.2 A$
- $R = 10\Omega$
- Now that you have the hang of it complete the practice problems.  
Attached



1. 5,700 Volts = \_\_\_\_\_ K Volts = \_\_\_\_\_ M Volts
2. 11 m Amp = \_\_\_\_\_ A = \_\_\_\_\_ u Amps
3. 2.5 Amps = \_\_\_\_\_ m Amps = \_\_\_\_\_ n Amps
4. 15 p Amps = \_\_\_\_\_ u Amps = \_\_\_\_\_ m Amps
5. .002 m Amps = \_\_\_\_\_ Amps = \_\_\_\_\_ u Amps

1. Using Ohm's Law, find V (in volts) when  $I = 1.25 \times 10^{-3}$  A and  $R = 2 \times 10^3 \Omega$ .
2. Using Ohm's Law, find R in kilohms when  $V = 12$  V and  $I = 25 \times 10^{-6}$  A.

The voltage across a resistor increases from 4.9 volts to 5.6 volts when the current is increased. What is the percent of increase in the voltage?

- Draw the CIRCUIT using computer simulation software.
- Show your MATH in the space provided.
- Label your answer.

1. A circuit has an applied voltage of 10 volts, and a resistance of 1,500 ohms. What is the current flowing in the circuit?

**Calculations**

$$V = \underline{\hspace{2cm}}$$

$$R = \underline{\hspace{2cm}}$$

$$I = \underline{\hspace{2cm}}$$

**Circuit**

**Answer:**                     

2. A circuit which contains 100 Kohms resistance has a current of 12 amperes. What is the applied voltage?

**Calculations**

$$V = \underline{\hspace{2cm}}$$

$$R = \underline{\hspace{2cm}}$$

$$I = \underline{\hspace{2cm}}$$

**Circuit**

**Answer:**                     

3. A circuit which contains 760 ohms resistance has a current flow of 20 ma. What is the applied emf - voltage?

**Calculations**

$$V = \underline{\hspace{2cm}}$$
$$R = \underline{\hspace{2cm}}$$
$$I = \underline{\hspace{2cm}}$$

**Circuit**

**Answer:**                     

4. A circuit has an applied voltage of 15 volts which causes 50 mA. of current to flow. What is the circuit's resistance?

**Calculations**

$$E = \underline{\hspace{2cm}}$$
$$R = \underline{\hspace{2cm}}$$
$$I = \underline{\hspace{2cm}}$$

**Circuit**

**Answer:**                     

5. An applied voltage of 10 volts causes a current of 5 uA to flow in the circuit. What is the total resistance in the circuit?

**Calculations**

$$E = \underline{\hspace{2cm}}$$
$$R = \underline{\hspace{2cm}}$$
$$I = \underline{\hspace{2cm}}$$

**Circuit**

**Answer:**                     

1. A circuit has an applied voltage of 5 volts which causes 30 ma. of current to flow. What is the circuit's resistance? Use Ohm's Law to find the correct resistance. Apply the 5 volts to the resistance on your breadboard and test for current.

Does the meter read 30ma?

2. A circuit has an applied voltage of 5 volts across a 360-ohm resistor. What is the circuit's current flow? Use Ohm's Law to find the correct current. Apply the 5 volts to the resistance on your breadboard and test for current.

Does the meter read the value you found using Ohm's Law?

## **Conclusion**

- 1) What are the circuit breakers in your house rated at? What do the breakers do?