



PLTW Engineering

10-12/Reading Electrical Schematics

4/14/2020



10-12/DE

Lesson: 4/14/2020

Objective/Learning Target: Students will be able to recognize and apply correct schematic symbols for electrical drawings




Symbols and what they mean

There are many different electrical symbols engineers and designers use to create blueprints for electrical circuits.

We need to be able to recognize the most common symbols and know what they mean.

Symbols and what they mean


The first group we will look at are analog symbols:

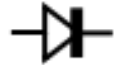 Diode

 Capacitor

 Inductor


 Resistor

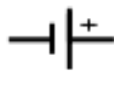 DC voltage
source

 AC voltage
source

Analog symbols


Diode

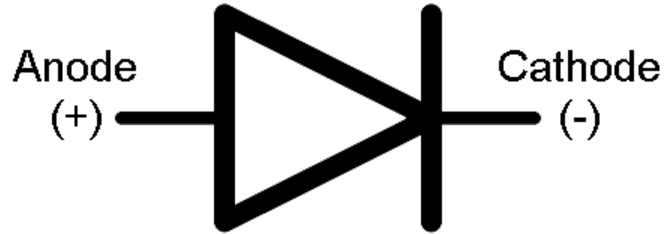

The diode allows current to flow in one direction but not backwards.

Analog symbols

Capacitor

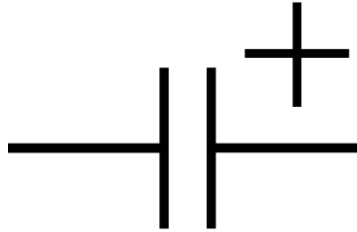

The capacitor stores electrical energy to be later discharged.

Analog symbols

Inductor



An inductor is sometimes referred to as a coil or choke. It stores energy in a magnetic field.

Analog symbols


Resistor



An resistor does just that - it resists current flow. It can also adjust signal levels, divide voltages, and bias active components.

Analog symbols


DC Voltage Source
(Direct Current)

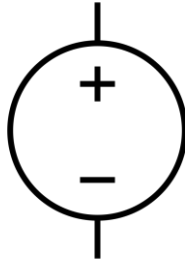

A DC voltage source is one that supplies and maintains a fixed output power level. An example would be a battery.







Analog symbols

AC Voltage Source
(Alternating Current)

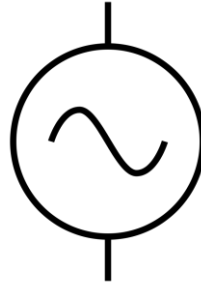


An AC voltage source is one that periodically changes polarity/direction between positive and negative.

Next, we will look at digital symbols:

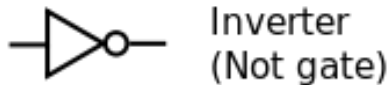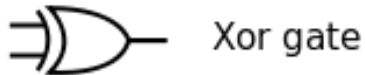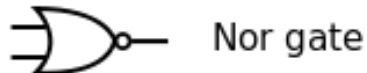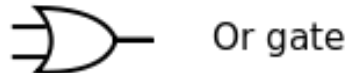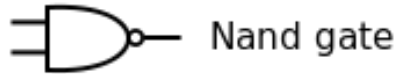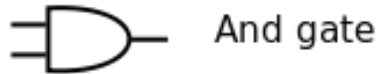

Digital Symbols

And gate

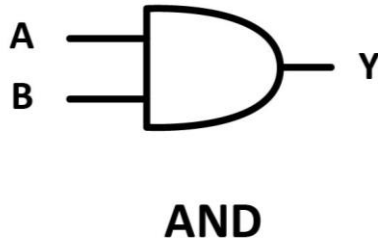


Inputs		Output
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table

The And gate is a digital gate with 2 inputs and one output. It behaves in accordance to the truth table at the right.

Digital Symbols

Nand gate

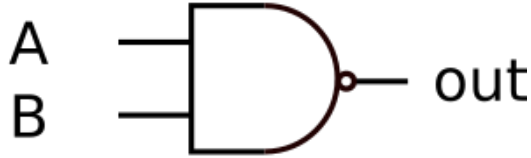

NAND:

A	B	out
0	0	1
0	1	1
1	0	1
1	1	0

The Nand gate is a digital gate with 2 inputs and one output. It behaves in accordance to the truth table at the right.

Or gate




A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

The Or gate is a digital gate with 2 inputs and one output. It behaves in accordance to the truth table at the right.

Digital Symbols


Nor gate

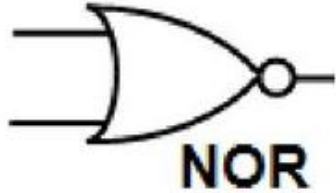

Inputs		Output
A	B	F
0	0	1
1	0	0
0	1	0
1	1	0

The Nor gate is a digital gate with 2 inputs and one output. It behaves in accordance to the truth table at the right.

Xor gate

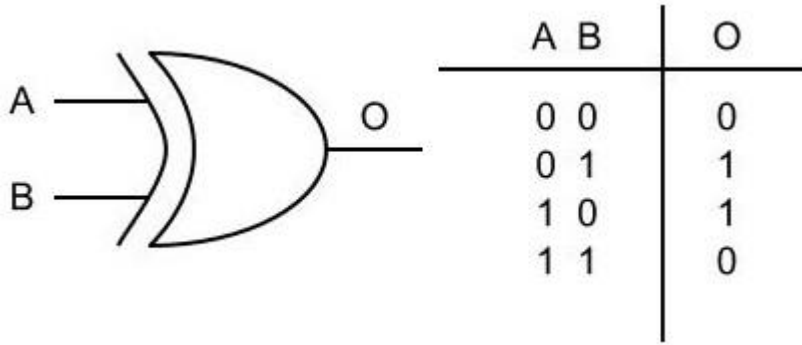


The Xor gate is a digital gate with 2 inputs and one output. It behaves in accordance to the truth table at the right.

Digital Symbols

Inverter gate

Symbol

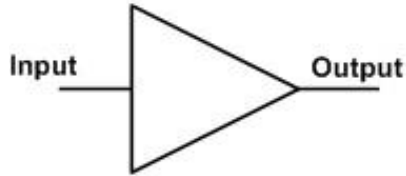


Truth Table

Input	Output
0	0
1	1

The Inverter gate is a digital gate with 1 input and 1 output. It behaves in accordance to the truth table at the right.

Additional symbols

Ground  The ground serves as a return path for current

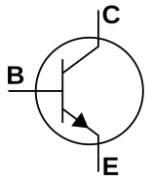Transistor  The transistor is used to amplify or switch power signals

LED  The light emitting diode is a low voltage bright light bulb

7 segment display  The seven segment display is a group of LEDs that can display a number.

Example electronic schematic

Take a look at the example circuit below and identify as many symbols as possible:

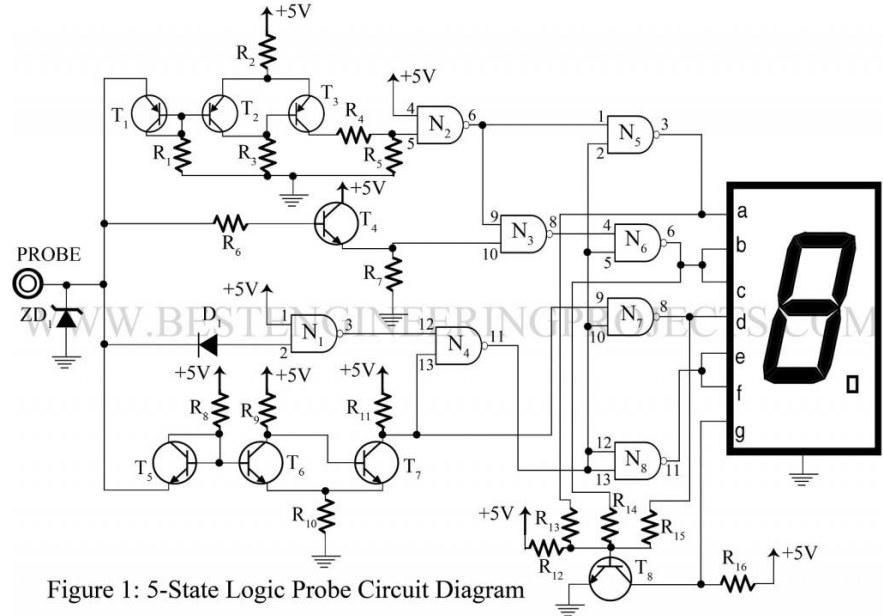


Figure 1: 5-State Logic Probe Circuit Diagram



Helpful Links

[Electronics Hub guide to schematics](#)

[Sparkfun guide to reading electrical schematics](#)