



PLTW Engineering

# 10-12/Advanced Parallel Circuit Calculations

April 22, 2020



10-12/DE

Lesson: **4/22/2020**

**Objective/Learning Target: Students will be able to calculate unknown resistance, current, or voltage values in a PARALLEL circuit with 3 or more components.**



## Review

In the previous lesson, we learned how to use Ohm's law to calculate unknown values in a very basic circuit.

However circuits have evolved over time and have become increasingly complex.

The following slides will show you how to calculate unknown resistance, current, or voltage values in a circuit with 3 or more components.



# Ohm's Law Review

## Ohms law review

$$V = I \times R$$


$$I = V / R$$

$$R = V / I$$
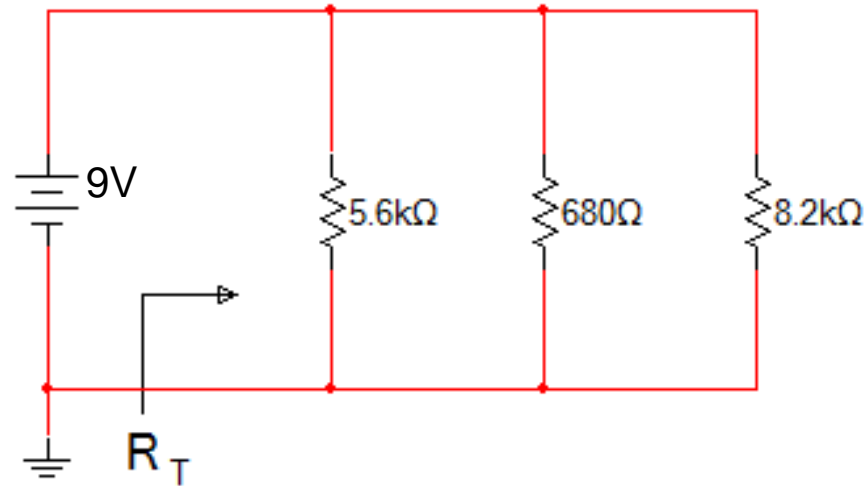
# Ohm's Law Total Resistance in Parallel

In the circuit shown to the right, we see there are 3 resistors in PARALLEL. In a parallel circuit, the reciprocal of the reciprocals of the resistor values are added together to determine the total resistance.

$$R_T = \frac{1}{\frac{1}{5.6k\Omega} + \frac{1}{680\Omega} + \frac{1}{8.2k\Omega}}$$




# Ohm's Law Total Resistance in Parallel

$$R_T = \frac{1}{\frac{1}{5.6\text{k}\Omega} + \frac{1}{680\Omega} + \frac{1}{8.2\text{k}\Omega}}$$

$$R_T = \frac{1}{.17857\Omega + .00147\Omega + .12195\text{k}\Omega}$$

$$R_T = \frac{1}{.3019912195}$$

$$R_T = 3.311 \text{ k}\Omega$$

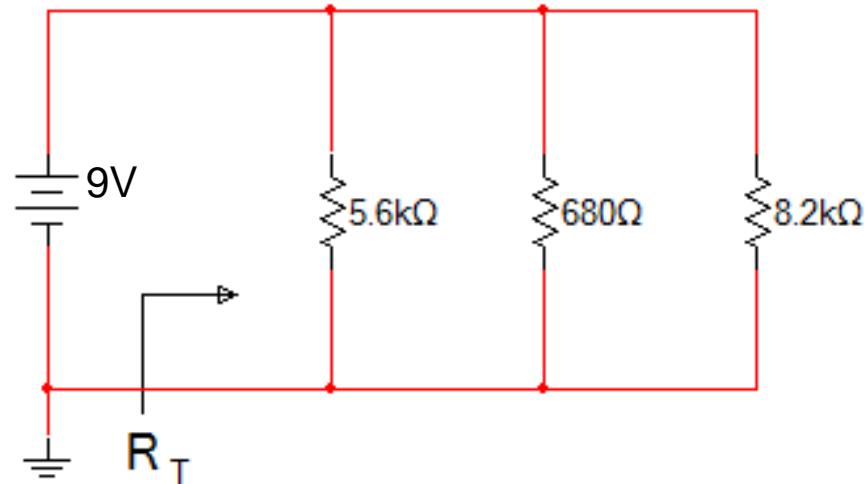

# Ohm's Law Total Current


With the total resistance calculated, we can now use Ohm's law to find the remaining unknown values.

$$R_T = 3.311\text{k}\Omega$$

$$I_T = V / R$$

$$I_T = 9\text{v} / 2,170\Omega$$


$$I_T = 2.72 \text{ mA}$$

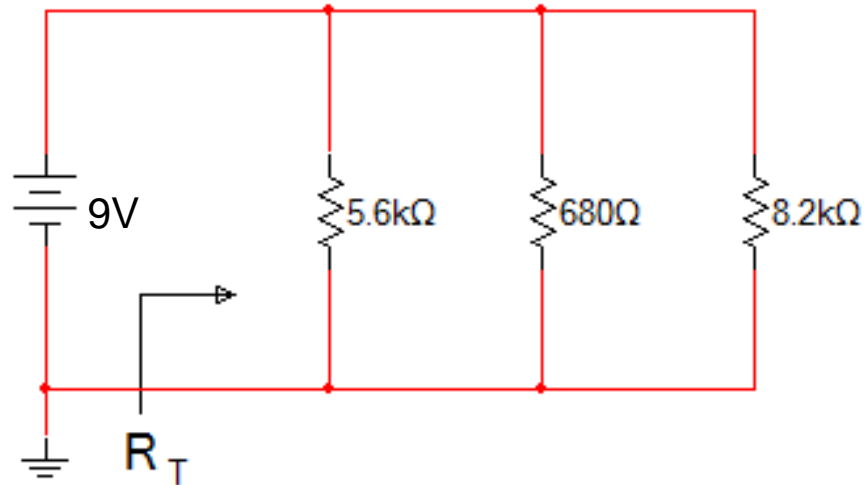
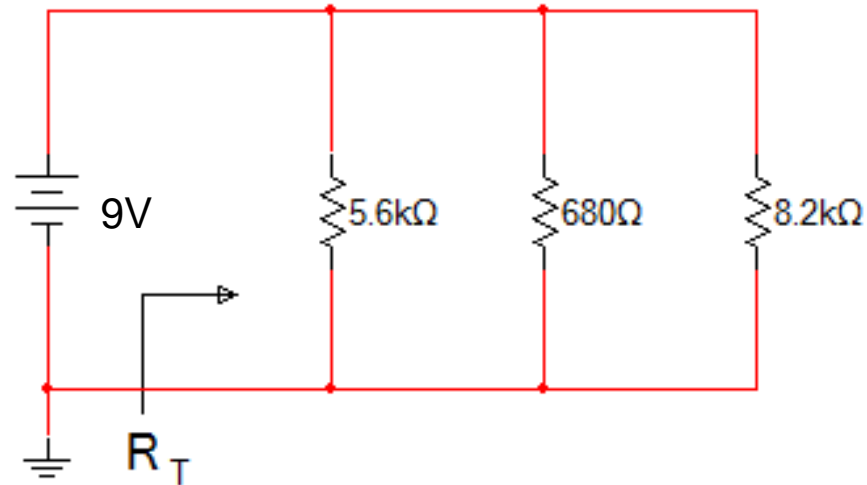
## Ohm's Law Advanced

With the total resistance and current calculated, we can calculate the current drops at each resistor. This is important when designing a circuit because it can help determine if a larger power source is needed.

$$R_T = 3.311\text{k}\Omega$$
$$I_T = 2.72\text{ mA}$$





# Ohm's Law Current Drops

$$I = V / R_1$$

$$I = 9\text{v} / 5.6\text{k}\Omega$$

$$I_{R1} = 1.6 \text{ k}\Omega$$

$$I = V / R_2$$


$$I = 9 \text{ v} / 680\Omega$$

$$I_{R2} = 0.013$$

$$I = V / R_3$$

$$I = 9 \text{ V} / 8.2\text{k}\Omega$$


$$I_{R3} = 1.09$$

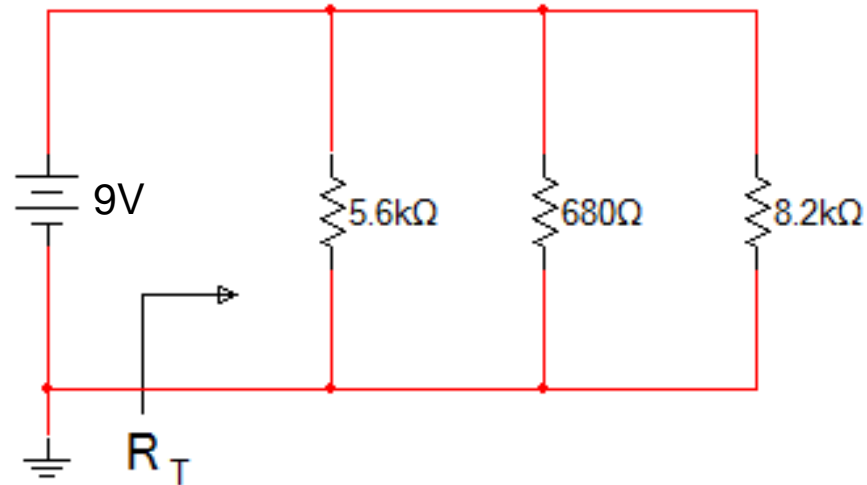
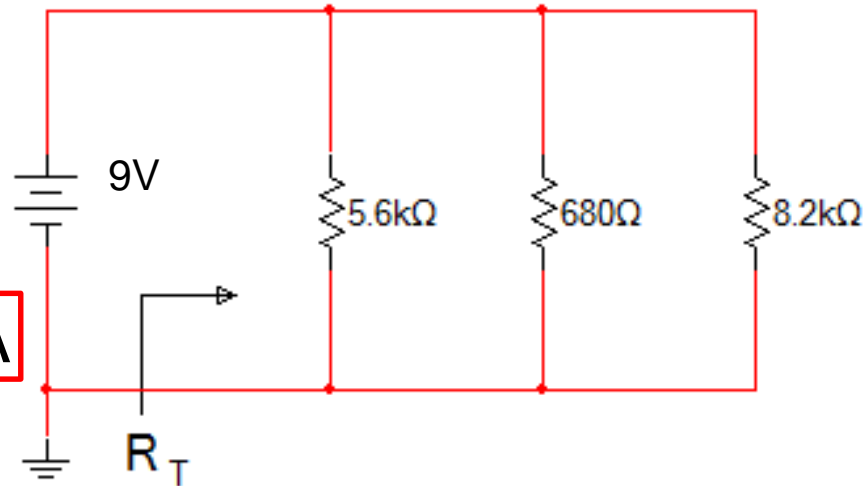
## Kirkchoff's Current Law

Now lets use Kirkchoff's current law we learned in the previous lesson to check our work. Remember, the total of all 3 current drops should add back up to current total - in this case approximately 2.72 mA.


$$\begin{aligned}
 & I_{R1} = 1.6 \text{ mA} \\
 + & I_{R2} = 0.013 \text{ mA} \\
 + & I_{R3} = 1.09 \text{ mA} \\
 & \quad \quad \quad = 2.703 \text{ mA}
 \end{aligned}$$



## Ohm's Law - Parallel Practice Problem

Here is a practice problem to try on your own. Remember the things you will need to calculate are as follows:

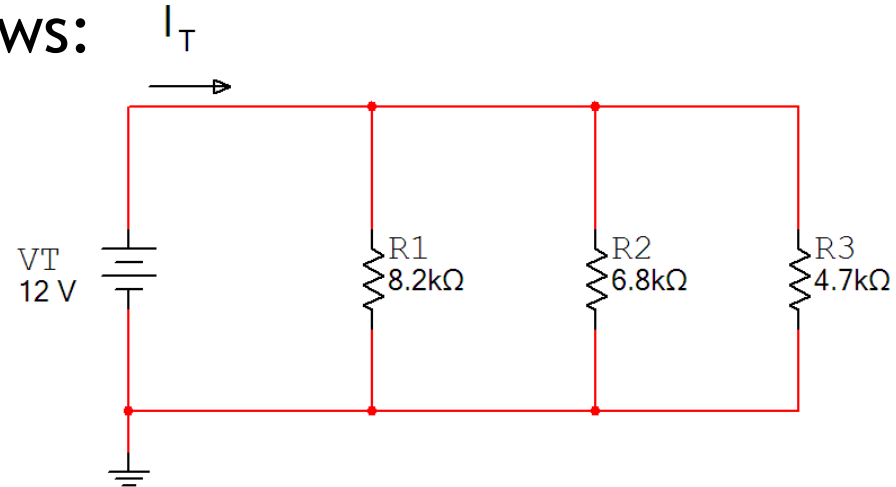1. Resistance total (parallel) -  $R_T$
2. Current total -  $I_T$  (mili Amps)
3. Current drops at each resistor  
 $I_{R1}$ ,  $I_{R2}$ ,  $I_{R3}$



4. Check your Current drops using Kirkchoff's current law



## Helpful links

[Youtube video - Solving a Parallel circuit tutorial](#)

[All about circuits guide to solving parallel circuits](#)