



PLTW Engineering

# 10-12/Advanced Series Circuit Calculations

April 23, 2020



10-12/DE

Lesson: **4/23/2020**

**Objective/Learning Target: Students will be able to calculate unknown resistance, current, or voltage values in a SERIES circuit with 3 or more components.**



## Review

In the previous lesson, we learned how to use Ohm's law to calculate unknown values in a very basic circuit.

However circuits have evolved over time and have become increasingly complex.

The following slides will show you how to calculate unknown resistance, current, or voltage values in a circuit with 3 or more components.



# Ohm's Law Review

## Ohms law review

$$V = I \times R$$


$$I = V / R$$

$$R = V / I$$
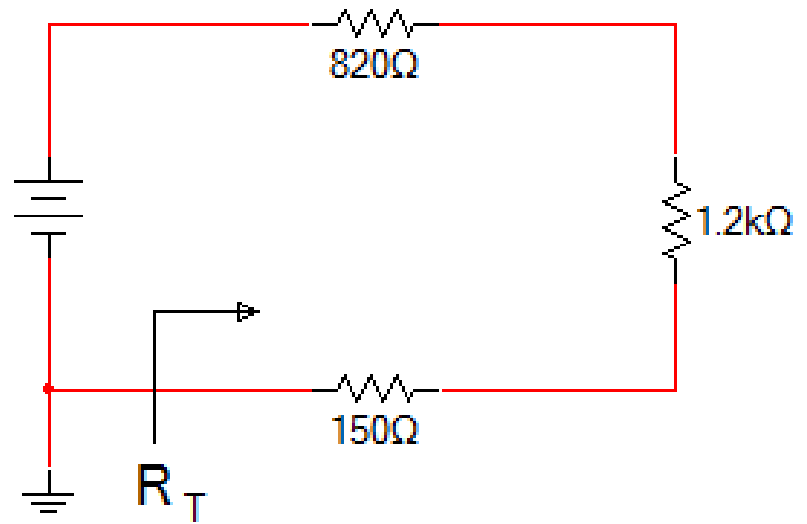
## Ohm's Law Resistance in Series

In the circuit shown to the right, we see there are 3 resistors in SERIES. In a series circuit, the resistors are added together to determine the total resistance.

$$\begin{array}{r} 820\Omega \\ 1200\Omega \\ + 150\Omega \\ \hline 2,170\Omega \text{ or } 2.17\text{k}\Omega \end{array}$$



## Ohm's Law Total Current


With the total resistance calculated, we can now use Ohm's law to find the remaining unknown values.

$$R_T = 2.17\text{k}\Omega$$

$$I_T = V / R$$

$$I_T = 9\text{v} / 2,170\Omega$$


$$I_T = 4.14 \text{ mA}$$

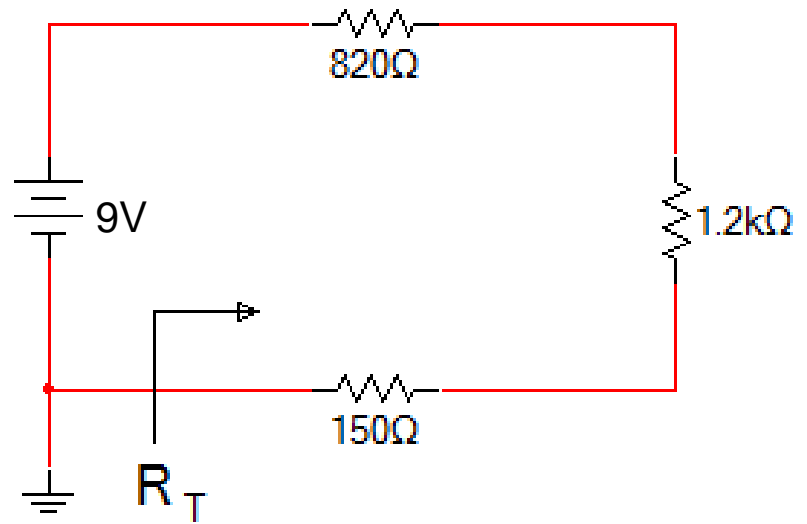
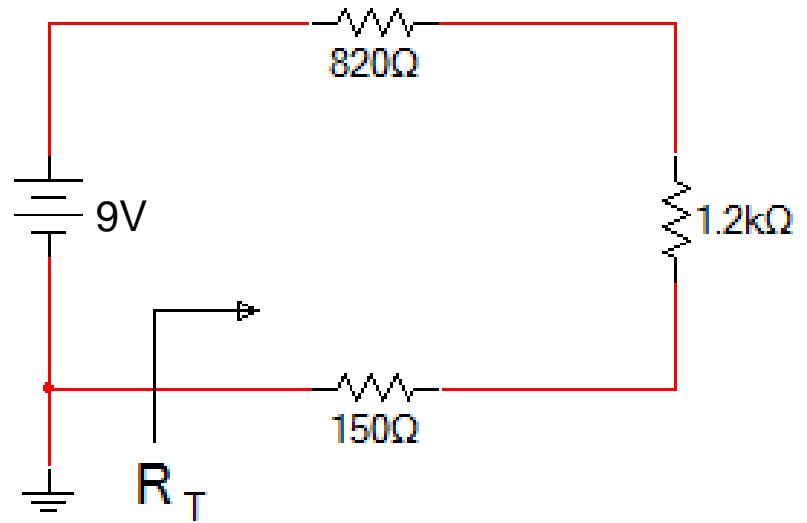
## Ohm's Law Advanced

With the total resistance and current calculated, we can calculate the voltage drops at each resistor. This is important when designing a circuit because it can help determine if a larger power source is needed.

$$R_T = 2.17\text{k}\Omega$$
$$I_T = 4.14\text{ mA}$$



# Ohm's Law Voltage Drops

$$V = I_T \times R_1$$

$$V = 4.14 \text{ mA} \times 820\Omega$$

$$V_{R1} = 3.39 \text{ V}$$

$$V = I_T \times R_2$$


$$V = 4.14 \text{ mA} \times 1.2\text{k}\Omega$$

$$V_{R2} = 4.99 \text{ V}$$

$$V = I_T \times R_3$$

$$V = 4.14 \text{ mA} \times 150\Omega$$

$$V_{R3} = 0.621 \text{ V}$$

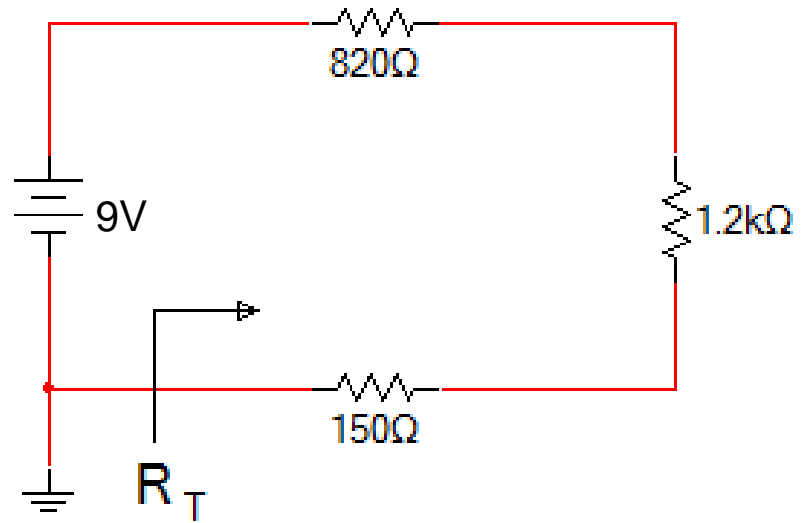



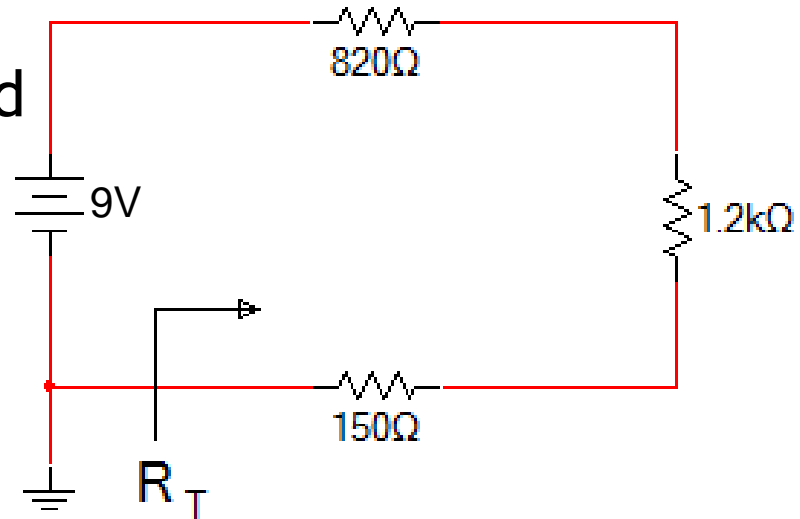
## Kirkchoff's Voltage Law

Now lets use Kirkchoff's voltage law we learned in the previous lesson to check our work. Remember, the total of all 3 voltage drops should add back up to source voltage - in this case 9v.


$$\begin{aligned}
 &V_{R1} = 3.39 \text{ V} \\
 + &V_{R2} = 4.99 \text{ V} \\
 + &V_{R3} = 0.621 \text{ V} \\
 &= 9.001 \text{ V}
 \end{aligned}$$



## Ohm's Law - Series Practice Problem

Here is a practice problem to try on your own. Remember the things you will need to calculate are as follows:

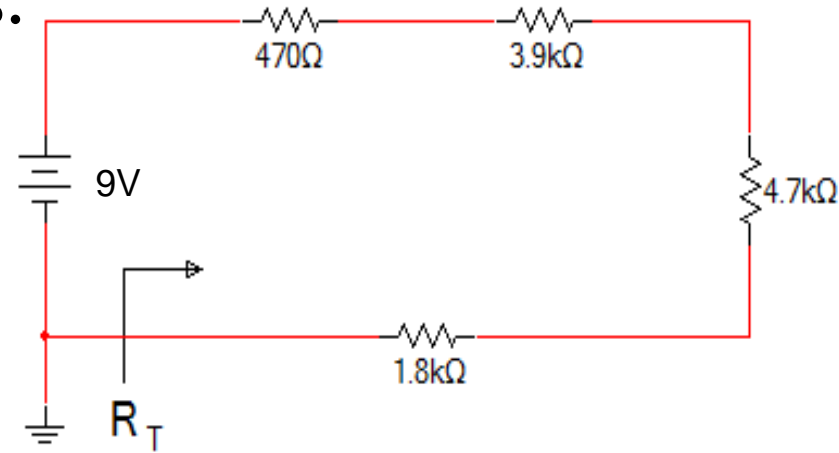1. Resistance total (series) -  $R_T$
2. Current total -  $I_T$  (mili Amps)
3. Voltage drops at each resistor  
 $V_{R1}$ ,  $V_{R2}$ ,  $V_{R3}$



4. Check your Voltage drops using Kirkchoff's voltage law



## Helpful links

[Youtube video - Series Circuit Calculation tutorial](#)

[All about circuits - Series Circuit Calculation examples](#)